 


Logic Design III

CSci 2021: Machine Architecture and Organization

With Slides from: Stephen McCamand, Ahmad Almulhem, and Hai Zhou

Bit Equality




`bool eq = (a&b) || (!a&!b)`

Generate 1 if a and b are equal

a	b	eq
0	0	1
0	1	0
1	0	0
1	1	1

Word Equality

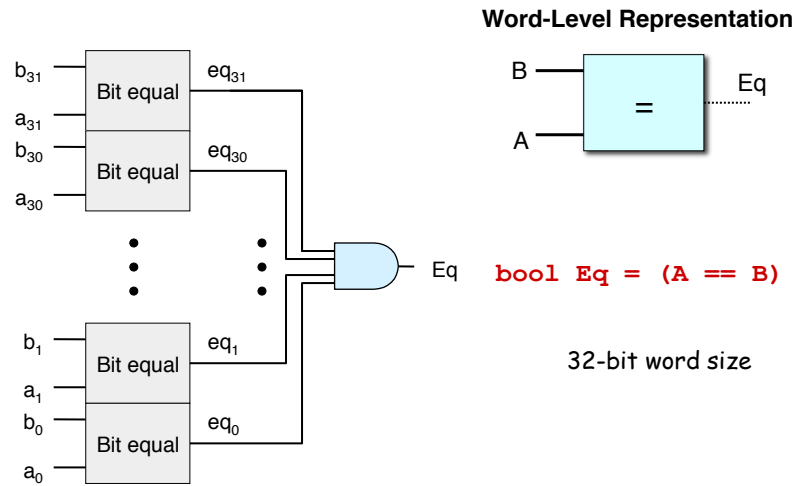

4/28/15

CSCI 2021

3

Decoder


4/29/15

CSCI 2021

UNIVERSITY OF MINNESOTA

4

Decoder

 

- Information is represented by binary codes
- **Decoding** - the conversion of an n -bit input code to an m -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code
- Circuits that perform decoding are called **decoders**


KFUPM

2-to-4 Decoder

- A 2-to-4 Decoder
 - 2 inputs (A_1, A_0)
 - $2^2 = 4$ outputs (D_3, D_2, D_1, D_0)

Truth Table


A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

KFUPM


2-to-4 Decoder with Enable

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

KFUPM


3-to-8 Decoder

 

A ₂	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


KFUPM

3-to-8 Decoder

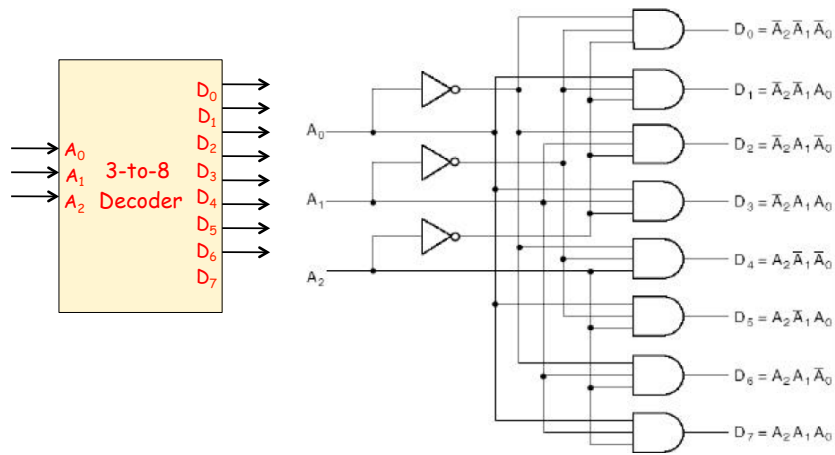

KFUPM


3-to-8 Decoder (using 2 2-to-4 decoders)

 

KFUPM

Encoder

Encoder

 

- **Encoding** - the opposite of decoding - the conversion of an m -bit input code to a n -bit output code with $n \leq m \leq 2^n$ such that each valid code word produces a unique output code
- Circuits that perform encoding are called **encoders**
- An encoder has 2^n (or fewer) input lines and n output lines which generate the binary code corresponding to the input values
- Typically, an encoder converts a code containing exactly one bit that is 1 to a binary code corresponding to the position in which the 1 appears.


8-to-3 Encoder

•Description:


• $2^3 = 8$ inputs, 3 outputs

•one input =1, others = 0's

•Each input generate unique binary code

 

8-to-3 Encoder (truth table)

 

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1


8-to-3 Encoder

•Description:


• $2^3 = 8$ inputs, 3 outputs

•one input =1, others = 0's

•Each input generate unique binary code

 

8-to-3 Encoder (truth table)

 

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

8-to-3 Encoder (truth table)

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

8-to-3 Encoder (truth table)

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	0	0	1	0	0
0	1	0	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

8-to-3 Encoder (truth table)

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

8-to-3 Encoder (equations)

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Output equations:

$A_0 = D_1 + D_3 + D_5 + D_7$

$A_1 = ?$

$A_2 = ?$

8-to-3 Encoder (equations)

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Output equations:

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = ?$$

8-to-3 Encoder (equations)

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1


Output equations:

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

8-to-3 Encoder (circuit)

 

Output equations:

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

8-to-3 Encoder (limitations)

Two Limitations:

1. Two or more inputs = 1

•Example: $D_3 = D_4 = 1$

• $A_2 A_1 A_0 = 111$

2. All inputs = 0

•Same as $D_0 = 1$

Output equations:

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

inputs								outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Priority Encoder


- Address the previous two limitations
 1. Two or more inputs = 1
 - Consider the bit with highest priority
 2. All inputs = 0
 - Add another output v to indicate this combination

Take Home Assignment

Multiplexer


Multiplexers

 - Is a combinational circuit
- Has a single output
- Directs one of 2^n input to the output
- Input to output direction is done based on a set of n select bits



Ahmad Almulhem,
KFUPM 2009

Bit-Level Multiplexor

 

- Control signal s
- Data signals a and b
- Output a when $s=1$, b when $s=0$

$$\text{bool out} = (s \& \& a) \mid \mid (!s \& \& b)$$


a	b	s	out
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

4/29/15


CSCI 2021



28

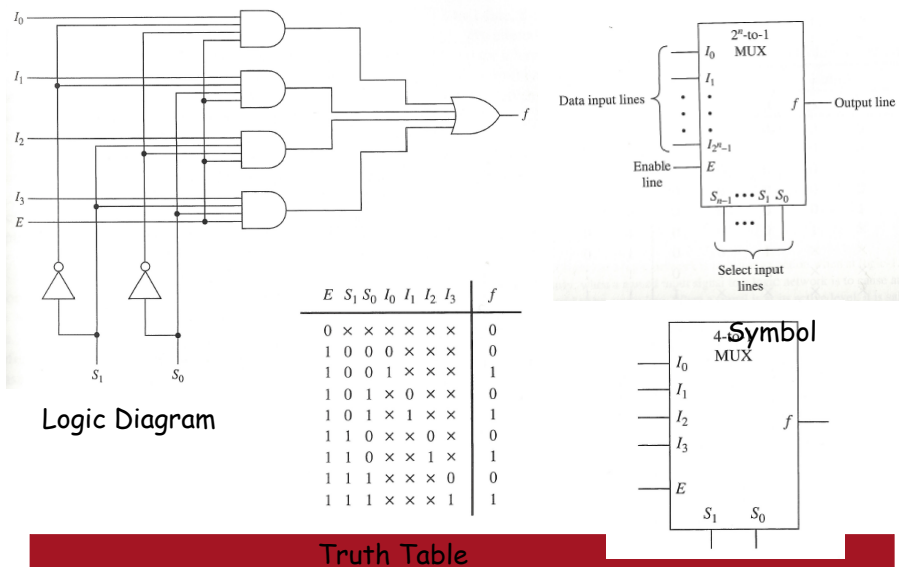Realization of 4-to-1 line multiplexer with enable




Building a Large Multiplexer

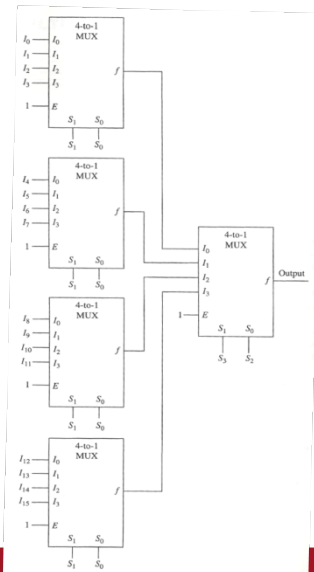

 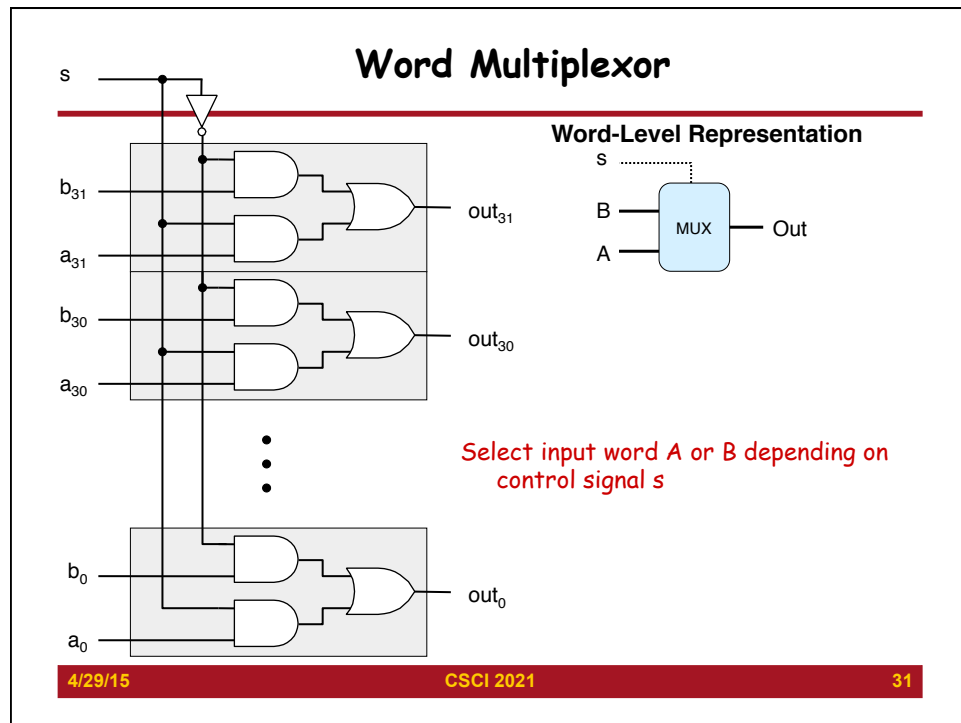


DeMultiplexer

 - Performs the inverse operation of a MUX
- It has one input and 2^n outputs
- The input is passed to one of the outputs based on the n select line



1x2 DeMUX

 

The circuit has an input E, the outputs are given by:


$$D_0 = E, \text{ if } S=0$$

$$D_1 = E, \text{ if } S=1$$

$$D_0 = S' E$$

$$D_1 = S E$$



1x4 DeMUX

 

The circuit has an input E, the outputs are given by:

$D_0 = E$, if $S_0S_1=00$	$D_0 = S_1'S_0' E$
$D_1 = E$, if $S_0S_1=01$	$D_1 = S_1'S_0 E$
$D_2 = E$, if $S_0S_1=10$	$D_2 = S_1S_0' E$
$D_3 = E$, if $S_0S_1=11$	$D_3 = S_1S_0 E$

DeMUX vs Decoder

  

- A 1x4 DeMUX is equivalent to a 2x4 Decoder with an Enable
 - Think of S_1S_0 as the decoder's input
 - Think of E as the decoder's enable
- In general, a DeMux is equivalent to a Decoder with an Enable

EN /E	A ₁ S ₁	A ₀ S ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

Adder

4/29/15 CSCI 2021

UNIVERSITY OF MINNESOTA

37

Adder

Carry In	→	0	0	0	0	1	1	1	1
Operand A	→	0	0	1	1	0	0	1	1
Operand B	→	+ 0	+ 1	+ 0	+ 1	+ 0	+ 1	+ 0	+ 1
		<u>0 0</u>	<u>0 1</u>	<u>0 1</u>	<u>1 0</u>	<u>0 1</u>	<u>1 0</u>	<u>1 0</u>	<u>1 1</u>
		↑↑							
Carry Out									
Sum									


Example:				
Carry	1	0	0	0
Operand A	0	1	0	0
Operand B	+ 0	1	1	0
Sum	<u>1</u>	<u>0</u>	<u>1</u>	<u>0</u>

4/28/15

CSCI 2021

Full Adder

A_i	B_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

4/28/15

CSCI 2021

39

Carry-In	A	B	Sum	Carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum} = A'BC' + AB'C' + A'B'C + ABC$$

$$\text{Carry-out} = ABC' + A'BC + AB'C + ABC$$


4/28/15

CSCI 2021

40

Four-Bit Ripple-Carry Adder

 - Four full adders connected in a ripple-carry chain form a four-bit ripple-carry adder.




4/28/15

CSCI 2021

41

Adder/Subtractor

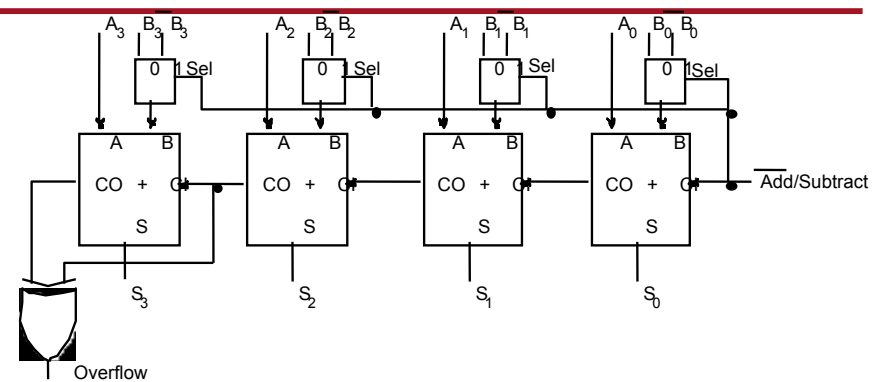

$$A - B = A + (-B) = A + \overline{B} + 1$$

42

Carry Lookahead Logic

Carry Generate $G_i = A_i B_i$ *must generate carry when $A = B = 1$*

Carry Propagate $P_i = A_i \text{ xor } B_i$ *carry in will equal carry out here*

Sum and Carry can be reexpressed in terms of generate/propagate:

$$S_i = A_i \text{ xor } B_i \text{ xor } C_i = P_i \text{ xor } C_i$$

$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$

$$= A_i B_i + C_i (A_i + B_i)$$

$$= A_i B_i + C_i (A_i \text{ xor } B_i)$$

$$= G_i + C_i P_i$$

43

Carry Lookahead Logic

Reexpress the carry logic as follows:

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$


$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

Each of the carry equations can be implemented in a two-level logic network

Variables are the adder inputs and carry in to stage 0!

44

Carry Lookahead Implementation

 


45

Multiplier

Theory of Multiplication

Basic Concept

 

47

Combinational Multiplier


Partial Product Accumulation

				A3	A2	A1	A0
				B3	B2	B1	B0
				A2 B0	A2 B0	A1 B0	A0 B0
		A3 B1	A2 B1	A1 B1	A0 B1		
	A3 B2	A2 B2	A1 B2	A0 B2			
	A3 B3	A2 B3	A1 B3	A0 B3			
S7	S6	S5	S4	S3	S2	S1	S0

48

Combinational Multiplier

Building block: full adder + and

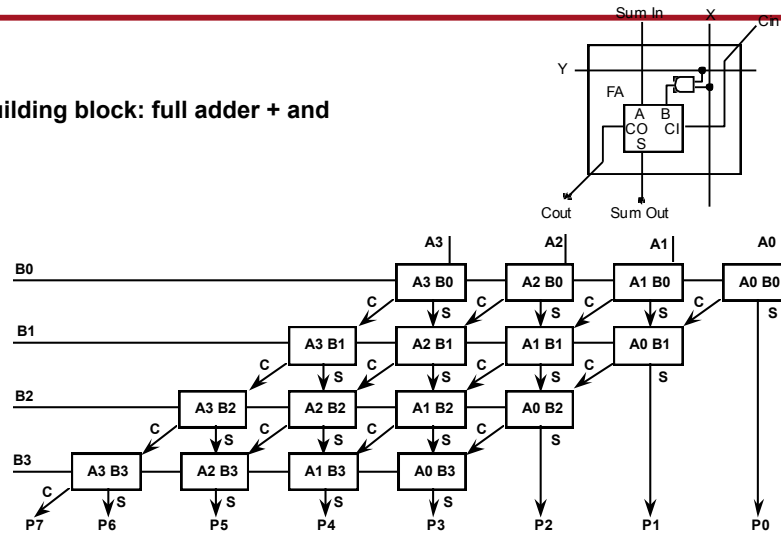

4 x 4 array of building blocks

49