

---

# Logic Design II

CSci 2021: Machine Architecture and Organization

With Slides from: Stephen McCamant, Xi Zhang and Hai Zhou

---

## Combinational Logic Design

---

- *Given*: description of circuit behavior
    - Word problem, or truth table
  - *Goal*: efficient circuit implementation
    - Usually most important: fewest gates and wires
    - Secondly: reduce number of levels (propagation delay)
  - *Kinds of techniques*
    - Up to 6 inputs: pencil and paper approaches
    - Large but structured: split into repeated pieces
    - Large and unstructured: computer algorithm
-

## DNF / SOP

- An input or its negation is called a *literal*
  - E.g.:  $a$ ,  $\neg b$
- An AND of literals is a *product term* or *cube*
  - E.g.:  $(a \ \& \ c)$ ,  $(a \ \& \ \neg b)$ ,  $(\neg a \ \& \ \neg b \ \& \ c)$ ,  $c$
- An OR of product terms is a *sum of products* (SOP), or in *disjunctive normal form* (DNF)
  - E.g.:  $(a \ \& \ b) \mid (a \ \& \ c)$
- (Dual: *product of sums* (POS), or *conjunctive normal form* (CNF))

## Inefficiency of Straight DNF

- Consider another example:

a	b	b
0	0	0
0	1	1
1	0	0
1	1	1

Result:  $(\neg a \ \& \ b) \mid (a \ \& \ b)$

- By algebra, can simplify back to "b"
  - Factor,  $(\neg a \mid a) = 1$ ,  $1 \ \& \ b = b$
- Can we recognize these patterns earlier?


## Karnaugh Map Idea

---

- Write truth table entries in an array
- Product terms represented by certain rectangles
- Visually, find small number of rectangles to cover 1 bits
  - OK to cover more than once, combine with OR
  - Fewer rectangles = smaller circuit

## 2-variable "Karnaugh Map"

---

 

## 2-variable "Karnaugh Map" example

Result:

$\neg a \mid b$

		$b =$	
		0	1
$a =$	0	1	1
	1	0	1

## Extending to 3 and 4 Variables

- Put two variables on a side
  - Weird order: 00 01 11 10
  - "Gray Code": change only one bit at a time
- Rectangles can enclose 1, 2, 4, or 8 entries
  - Bigger is better
- Rectangles can wrap around the edges
  - 00 is adjacent to 10


## 4-variable Karnaugh Map Example

		ab =				
		00	10	11	01	
cd =	00	0	1	0	1	(a & !b)
	10	0	1	0	0	(a & d)
	11	0	1	1	0	(!a & b
	01	0	1	1	0	& !c & !d)

## Extending to 5 and 6 Variables

- 2D is no longer enough
  - No way to order 3 variables to capture 12 adjacencies
- Approach: stacking
  - Make 2 (for 5 inputs) or 4 (for 6 inputs) 4-input Karnaugh maps
  - Corresponding entries are "on top of" each other
  - Rectangles become 3D
  - Usually still drawn as 2D
  - With 6, more possibilities for wrapping too

## 5-variable Karnaugh Map Example

 

0	1	0	1
0	1	0	0
0	1	1	0
0	1	1	0

0	0	0	1
0	0	0	0
0	1	1	0
0	1	1	0

## Karnaugh Map Tips: Overlap is Good

		ab =			
		00	10	11	01
cd =	00	0	1	0	0
	10	0	1	0	0
	11	0	1	1	0
	01	0	1	1	0

### Karnaugh Map Tips: No 3s

cd =

		00	10	ab = 11	01
00		0	0	0	0
10		0	1	0	0
11		0	1	0	0
01		0	1	0	0

### Karnaugh Map Tips: Wrap Around

cd =

		00	10	ab = 11	01	
00		1	0	0	1	!a & !c
10		0	0	0	0	
11		0	0	0	0	
01		1	0	0	1	

## Don't Cares

- Some results don't matter
  - Domain of function is a subset of all n-bit strings
  - Unused bit patterns in encodings
  - Bits sometimes ignored by other circuits
- "Don't care" value could be 0 or 1
  - Usually denoted by X
- Don't-cares allow designs to be simpler
  - Choose the value that allows a simpler circuit
- In early CPUs, led to undocumented instructions
  - Example: x86 ASL vs. SHL
  - On modern CPUs, more error checking

## Karnaugh Map Tips: Don't Cares


ab =

	00	10	11	01
00	X	0	X	1
10	0	X	X	X
11	X	X	X	X
01	1	X	X	X

cd =




## Dual (POS) Karnaugh Maps

 


## Case Study of a Simple Logic Design: Seven Segment Display

- Chip to drive digital display

 


B3	B2	B1	B0	Val
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9

## Case Study (cont.)

 

B3	B2	B1	B0	Val	L1	L2	L3	L4	L5	L6	L7
0	0	0	0	0	1	0	1	1	1	1	1
0	0	0	1	1	0	0	0	0	0	1	1
0	0	1	0	2	1	1	1	0	1	1	0
0	0	1	1	3	1	1	1	0	0	1	1
0	1	0	0	4	0	1	0	1	0	1	1
0	1	0	1	5	1	1	1	1	0	0	1
0	1	1	0	6	1	1	1	1	1	0	1
0	1	1	1	7	1	0	0	0	0	1	1
1	0	0	0	8	1	1	1	1	1	1	1
1	0	0	1	9	1	1	1	1	0	1	1

 

## Case Study (cont.)

- Implement L4:

Boolean function for L4

B3	B2	B1	B0	L4
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1

$B1B0$     00    10    11    01  
 $B3B2$   
 00  
 10  
 11  
 01

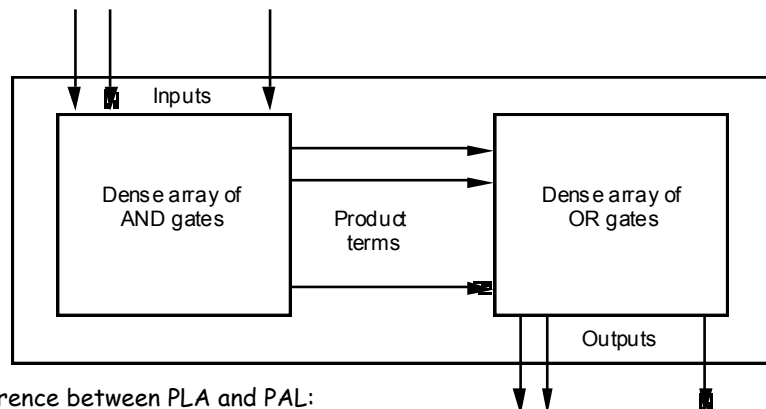

## ASIC vs. Programmable Logic Device

- PLDs programmable logic devices
  - Simple PLD (SPLD)
    - Programmable logic array (PLA)
    - Programmable array logic (PAL)
  - Complex PLD (CPLD)
  - Field-programmable gate arrays (FPGA)
- ASICs
  - application specific integrated circuits

## PALs and PLAs

Pre-fabricated building block of many AND/OR gates (or NOR, NAND)  
"Personalized" by making or breaking connections among the gates

*Programmable Array Block Diagram for Sum of Products Form*




Difference between PLA and PAL:


**PLA:** both AND plane and OR plane are programmable.

**PAL:** Only AND plane is programmable, while OR plane is fixed.


## Example of PALs and PLAs

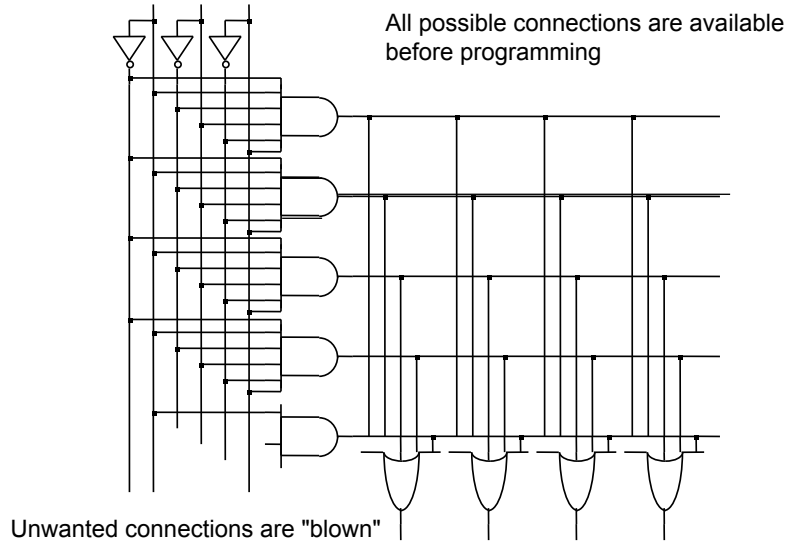

## Alternative Representations


 


 Short-hand notation  
so we don't have to  
draw all the wires!



Notation for implementing  
 $F0 = AB + A'B'$   
 $F1 = CD' + C'D$

## Design Example

  

## Automated Methods

- Karnaugh maps don't scale well beyond 6 inputs
- Good job for a computer!
- Quine-McCluskey algorithm
  - Tabular analog to Karnaugh maps
  - Optimal, but suffers from exponential blowup
- Heuristic methods like "espresso"
  - First, greedily achieve coverage
  - Then, opportunistically improve
  - No optimality guarantee, but good scalability
- Now a standard part of CAD systems
  - Like compilers for software