

CSci 2021, Spring 2015

Homework Assignment V: Solutions

Problem 0: (1 point)

Should have been easy.

Problem 1:

$$f_1 = (b \wedge (a \& c)) \& (a \mid c)$$

a	b	c	a & c	b \wedge (a&c)	a \mid c	f_1
0	0	0	0	0	0	0
0	0	1	0	0	1	0
0	1	0	0	1	0	0
0	1	1	0	1	1	1
1	0	0	0	0	1	0
1	0	1	1	1	1	1
1	1	0	0	1	1	1
1	1	1	1	0	1	0

$$f_2 = ((a \& b) \wedge c) \& (b \mid (a \wedge b))$$

a	b	c	a & b	(a&b) \wedge c	a \wedge b	b \mid (a \wedge b)	f_2
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	0	0	1	1	0
0	1	1	0	1	1	1	1
1	0	0	0	0	1	1	0
1	0	1	0	1	1	1	1
1	1	0	1	1	0	1	1
1	1	1	1	0	0	1	0

Problem 2:

x_1x_0	y_1y_0	$z_3z_2z_1z_0$
00 (0)	00 (0)	0000 (0)
00 (0)	01 (1)	0000 (0)
00 (0)	10 (-2)	0000 (0)
00 (0)	11 (-1)	0000 (0)
01 (1)	00 (0)	0000 (0)
01 (1)	01 (1)	0001 (1)
01 (1)	10 (-2)	1110 (-2)
01 (1)	11 (-1)	1111 (-1)
10 (-2)	00 (0)	0000 (0)
10 (-2)	01 (1)	1110 (-2)
10 (-2)	10 (-2)	0100 (4)
10 (-2)	11 (-1)	0010 (2)
11 (-1)	00 (0)	0000 (0)
11 (-1)	01 (1)	1111 (-1)
11 (-1)	10 (-2)	0010 (2)
11 (-1)	11 (-1)	0001 (1)

		x_1x_0			
z_0		00	01	11	10
	00	0	0	0	0
	01	0	1	1	0
y_1y_0	11	0	1	1	0
	10	0	0	0	0

$$z_0 = x_0 \& y_0$$

		x_1x_0			
z_1		00	01	11	10
	00	0	0	0	0
	01	0	0	1	1
y_1y_0	11	0	1	0	1
	10	0	1	1	0

$$z_1 = (x_1 \& !y_1 \& y_0) | (y_1 \& !x_1 \& x_0) | (y_0 \& x_1 \& !x_0) | (x_0 \& y_1 \& !y_0)$$


		x_1x_0			
z_2		00	01	11	10
	00	0	0	0	0
	01	0	0	1	1
y_1y_0	11	0	1	0	0
	10	0	1	0	1

$$z_2 = (x_1 \& !y_1 \& y_0) | (y_1 \& !x_1 \& x_0) | (x_1 \& !x_0 \& y_1 \& !y_0)$$

		x_1x_0			
z_3		00	01	11	10
	00	0	0	0	0
	01	0	0	1	1
y_1y_0	11	0	1	0	0
	10	0	1	0	0

$$z_3 = (x_1 \& !y_1 \& y_0) | (y_1 \& !x_1 \& x_0)$$


Problem 3:

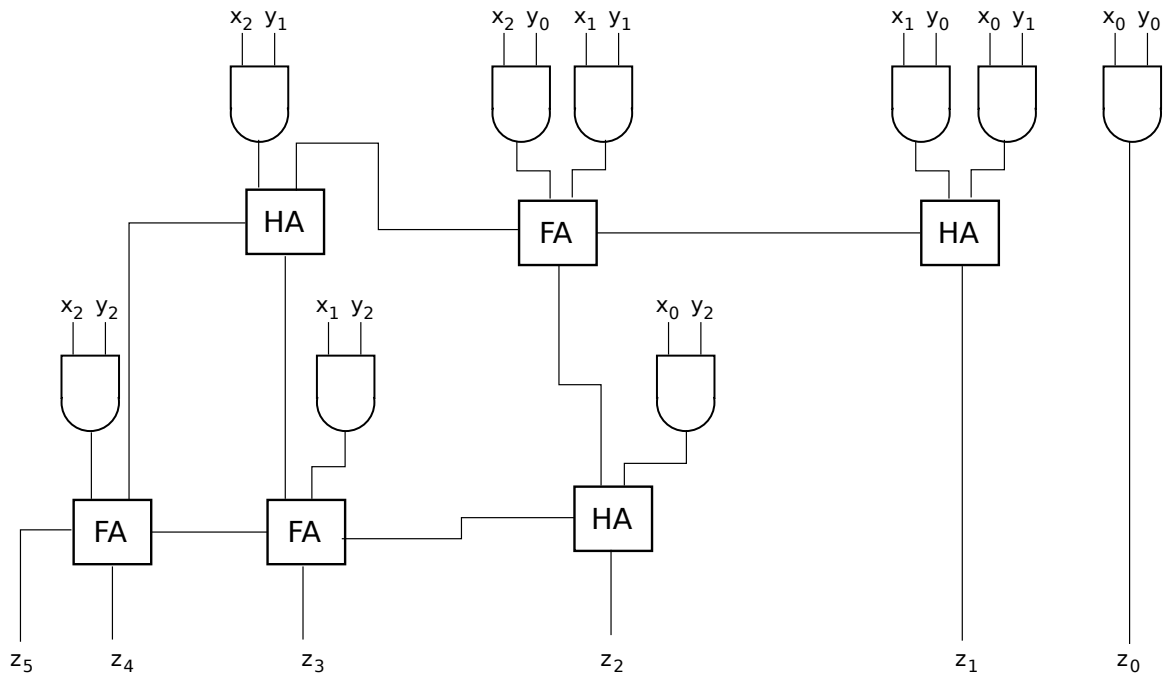

Problem 4:

- a. One way of writing the update function for the HSRLTD flip-flop is:

$$Q^+ = !R \& ((H \& Q) | S | (L \& (D \wedge T)) | (T \& !L \& !Q))$$

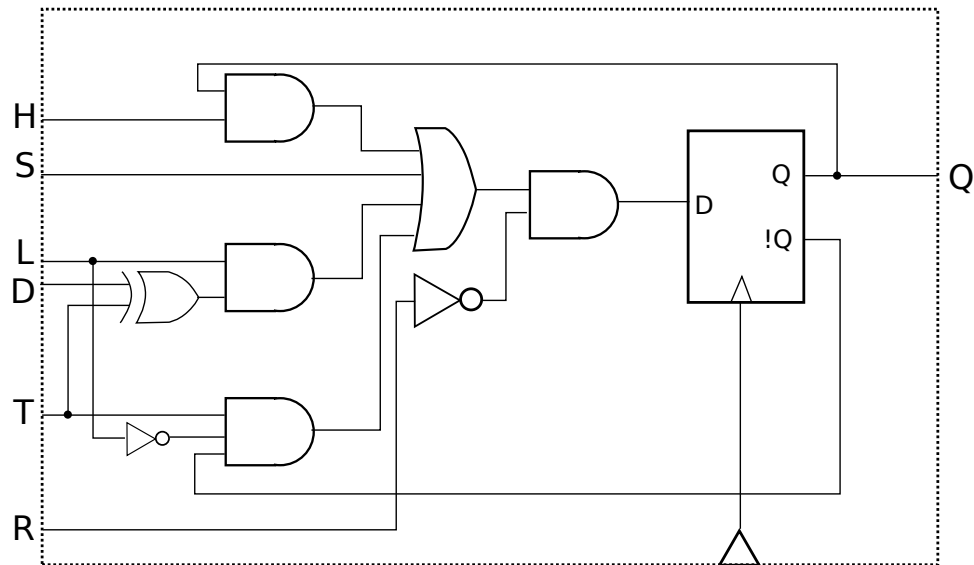

This is not an ideal place to use a Karnaugh map, because if you include the 5 control signals plus D and Q, there are 7 inputs. But you could make a 5-input map based on just the control signals, by putting D and Q expressions in the map:


		SR						SR			
		00	01	11	10			00	01	11	10
HT	L = 0	X	0	X	1	HT	L = 1	D	X	X	X
		!Q	X	X	X			!D	X	X	X
		X	X	X	X			X	X	X	X
		Q	X	X	X			X	X	X	X

This gives the following alternative formula:

$$Q^+ = (H \& Q) | S | (L \& (D \wedge T)) | (T \& !L \& !Q)$$

which shows that the R input is not actually needed.

- b. The JK inputs 00, 01, 10, and 11 correspond to the HSRLTD signals H, R, S, and T respectively, so this a good job for a 2:4 decoder.

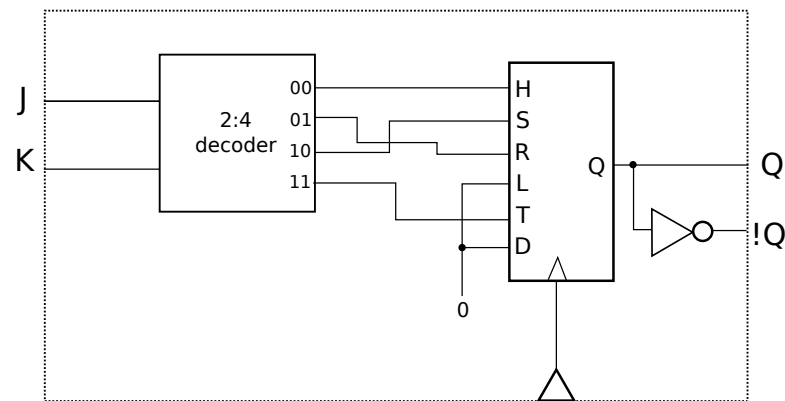

Problem 5:

a.

z_0

	x_3x_2				
	00	01	11	10	
x_1x_0	00	1	1	X	1
	01	0	0	X	0
	11	0	0	X	X
	10	1	1	X	X

$z_0 = !x_0$

z_1

	x_3x_2				
	00	01	11	10	
x_1x_0	00	0	0	X	0
	01	1	1	X	0
	11	0	0	X	X
	10	1	1	X	X

$z_1 = (!x_3 \& !x_1 \& x_0) | (x_1 \& !x_0)$

z_2


	x_3x_2				
	00	01	11	10	
x_1x_0	00	0	1	X	0
	01	0	1	X	0
	11	1	0	X	X
	10	0	1	X	X

$z_2 = (x_2 \& !x_1) | (!x_2 \& x_1 \& x_0) | (x_2 \& x_1 \& !x_0)$

z_3

	x_3x_2				
	00	01	11	10	
x_1x_0	00	0	0	X	1
	01	0	0	X	0
	11	0	1	X	X
	10	0	0	X	X


$z_3 = (x_3 \& !x_1) | (x_2 \& x_1 \& x_0)$

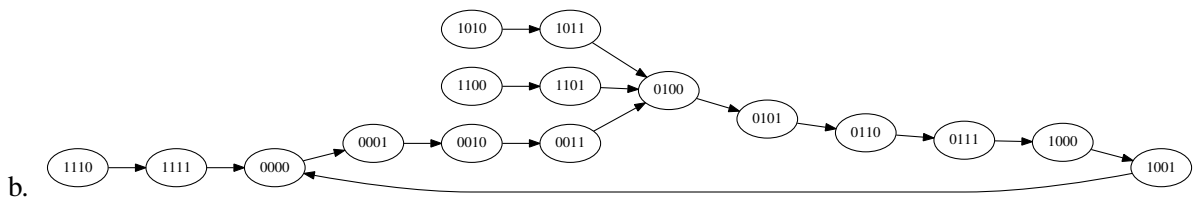

Since every path leads to the main cycle, this design is self-starting.

Problem 6:

a.

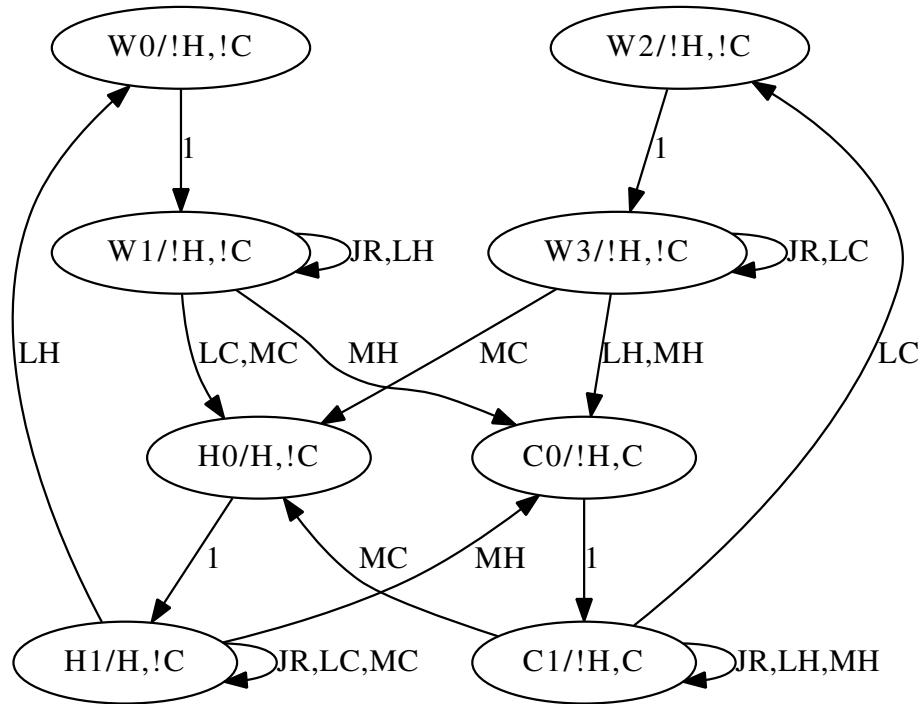

b. State encoding and output:

State	Q_0	Q_1	Q_2	H	C
W_0	0	0	0	0	0
W_1	0	0	1	0	0
W_2	0	1	0	0	0
W_3	0	1	1	0	0
C_0	1	0	0	0	1
C_1	1	0	1	0	1
H_0	1	1	0	1	0
H_1	1	1	1	1	0

State transition function. Note that rows with a don't-care X in one of the T columns abbreviate a sequence of rows with the same output that differ only in those positions.

Label	Q_0	Q_1	Q_2	T_g	T_h	T_b	Q'_0	Q'_1	Q'_2
$W_0 \rightarrow W_1$	0	0	0	X	X	X	0	0	1
$W_1 \rightarrow H_0$	0	0	1	0	0	X	1	1	0
$W_1 \rightarrow W_1$	0	0	1	0	1	0	0	0	1
$W_1 \rightarrow C_0$	0	0	1	0	1	1	1	0	0
$W_1 \rightarrow W_1$	0	0	1	1	X	X	0	0	1
$W_2 \rightarrow W_3$	0	1	0	X	X	X	0	1	1
$W_3 \rightarrow W_3$	0	1	1	0	0	0	0	1	1
$W_3 \rightarrow H_0$	0	1	1	0	0	1	1	1	0
$W_3 \rightarrow C_0$	0	1	1	0	1	X	1	0	0
$W_3 \rightarrow W_3$	0	1	1	1	X	X	0	1	1
$C_0 \rightarrow C_1$	1	0	0	X	X	X	1	0	1
$C_1 \rightarrow W_2$	1	0	1	0	0	0	0	1	0
$C_1 \rightarrow H_0$	1	0	1	0	0	1	1	1	0
$C_1 \rightarrow C_1$	1	0	1	0	1	X	1	0	1
$C_1 \rightarrow C_1$	1	0	1	1	X	X	1	0	1
$H_0 \rightarrow H_1$	1	1	0	X	X	X	1	1	1
$H_1 \rightarrow H_1$	1	1	1	0	0	X	1	1	1
$H_1 \rightarrow W_0$	1	1	1	0	1	0	0	0	0
$H_1 \rightarrow C_0$	1	1	1	0	1	1	1	0	0
$H_1 \rightarrow H_1$	1	1	1	1	X	X	1	1	1