

Logic Design V

CSCI 2021: Machine Architecture and Organization

Antonia Zhai

Department Computer Science and Engineering

University of Minnesota

<http://www.cs.umn.edu/~zhai>


With Slides from Hai Zhou Stephen McCamant and Wei-Chung Hsu

UNIVERSITY OF MINNESOTA

JK Latch Design

How to eliminate the forbidden state?

J(t)	K(t)	Q(t)	Q(t+d)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

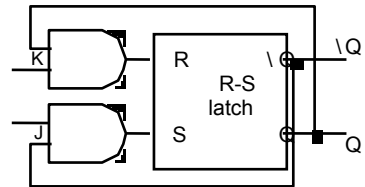


Idea: use output feedback to guarantee that R and S are never both one

J, K both one yields toggle

Characteristic Equation:

$$Q^+ = Q\bar{K} + \bar{Q}J$$


J-K Flip-Flop

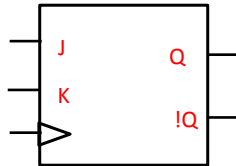

- More powerful input type
 - Like combination of S-R and T
- Cases:
 - $J = K = 0$: no change
 - $J = 1$: set; $K = 1$: reset
 - $J = K = 1$: toggle
- $Q' = (Q \& !K) \mid (!Q \& J)$

Take Home: How to design an edge-triggered JK flip-flop?

T Flip-Flop

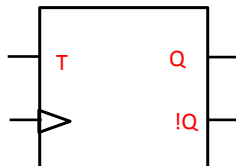


- Another input style, $T = \text{"toggle"}$
- Flip-flop behavior summarized by state update formula
 - Here, $Q' = (Q \wedge T)$
 - $T = 0$: unchanged; $T = 1$: value is negated

Build a T Flip-Flop from a JK Flip-Flop

Shift Register

- Flip-flops connected in series
- Behavior:
 - Sequence of bits each move one stage per clock cycle
- Variations:
 - Serial or parallel input
 - Series or parallel output
 - Shift only on some cycles

How to support parallel input?

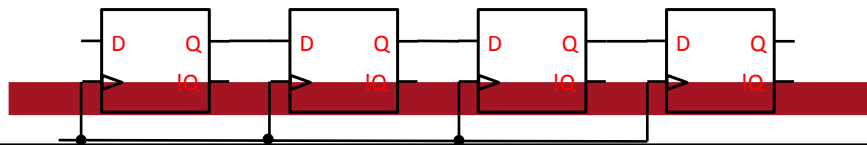


Counters

- Simple kind of time-varying digital system
 - Produces a single sequence of states, repeating
 - Changes every cycle or on a count pulse
- Example: 3-bit binary up-counter
 - Produces 000, 001, 010, 011, 100, 101, 110, 111, 000, 001, ...
- Variations:
 - Down-counters
 - Decade counters (for decimal): 0 through 9
 - Gray code: sequence where only one bit changes at a time
 - Ring counter: circular shift register producing one-hot outputs

Counter Design

Step 1: Derive the State Transition Diagram

Count sequence: 000, 010, 011, 101, 110

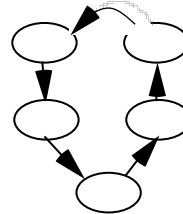


Present State	Next State
000	010
010	011
011	101
101	110
110	000

Step 2: State Transition Table




7

Implementing 5-state counter with D FFs

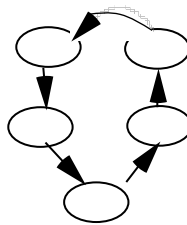Continuing with the 000, 010, 011, 101, 110,



Present State	Next State
A B C	D _A D _B D _C
000	010
001	X X X
010	011
011	101
100	X X X
101	110
110	000
111	X X X

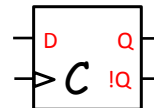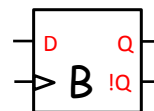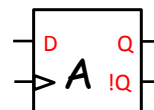

A

Implementing 5-state counter with RS FFs

Continuing with the 000, 010, 011, 101, 110

	Present State			Next State		
	C	B	A	D _C	D _B	D _A
0	0	0	0	0	1	0
0	0	0	1	X	X	X
0	0	1	0	0	1	1
0	0	1	1	1	0	1
1	1	0	0	X	X	X
1	1	0	1	1	1	0
1	1	1	0	0	0	0
1	1	1	1	X	X	X

D_C

A\BC	00	01	11	10
0	0	X	0	0
1	X	1	X	1

D_B

A\BC	00	01	11	10
0	1	X	0	1
1	X	1	X	0

D_A


A\BC	00	01	11	10
0	0	X	0	1
1	X	0	X	1

Implementing 5-state counter with D FFs

$$D_C = A$$

$$D_B = A' C' + B'$$

$$D_A = B C'$$

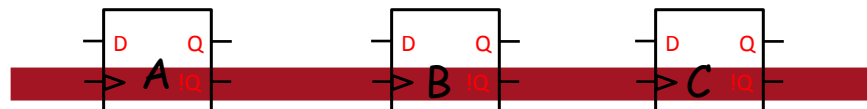

Implementing 5-state counter with RS FFs

Continuing with the 000, 010, 011, 101, 110

	R	S	Present State	Next State	Remapped next state					
					RC	SC	RB	SB	RA	SA
0 0	X	0	000	010	X	0	0	1	X	0
0 1	0	1	001	XXX	X	X	X	X	X	X
1 0	1	0	010	011	X	0	0	X	0	1
1 1	0	X	011	101	0	1	1	0	0	X
			100	XXX	X	X	X	X	X	X
			101	110	0	X	0	1	1	0
			110	000	1	0	1	0	X	0
			111	XXX	X	X	X	X	X	X

$$Q^+ = S + R \bar{Q}$$

11

Remapped Next State Functions

Implementation with RS FFs

RS FFs Continued

A \ CB	00	01	11	10
0	X	X	1	X
1	X	0	X	0

RC

A \ CB	00	01	11	10
0	0	0	0	X
1	X	1	X	X

SC

$$RC = \bar{A}$$

$$SC = A$$

A \ CB	00	01	11	10
0	0	0	1	X
1	X	1	X	0

RB

A \ CB	00	01	11	10
0	1	X	0	X
1	X	0	X	1

SB

$$RB = AB + BC$$

$$SB = \bar{B}$$

$$RA = C$$

$$SA = B \bar{C}$$

A \ CB	00	01	11	10
0	X	0	X	X
1	X	0	X	1

RA

A \ CB	00	01	11	10
0	0	1	0	X
1	X	X	X	0

SA

12

Basic Design Approach

1. Understand the statement of the Specification
2. Obtain an abstract specification of the FSM
3. Perform a state minimization
4. Perform state assignment
5. Choose FF types to implement FSM state register
6. Implement the FSM

13

Example: Vending Machine FSM

deliver package of gum after 15 cents deposited


single coin slot for dimes, nickels

no change

Step 1. *Understand the problem:*

Draw a picture!

Block Diagram

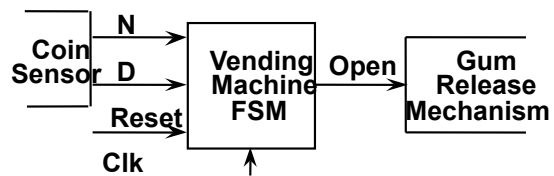

14

Vending Machine Example

Step 2. Map into more suitable abstract representation


Tabulate possible input sequences:

three nickels
nickel, dime
dime, nickel
two dimes
two nickels, dime

Draw state diagram:

Inputs: N, D, reset


Output: open

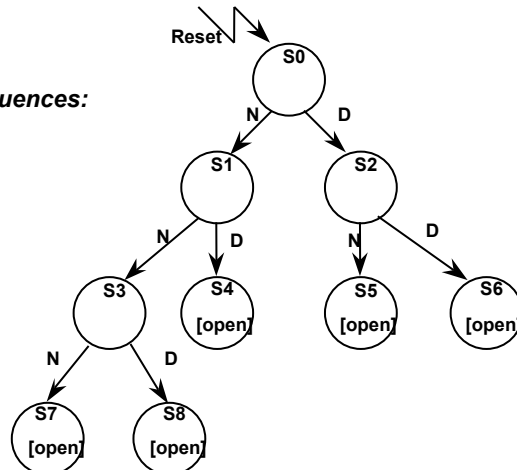

15

Vending Machine Example

Step 3: State Minimization

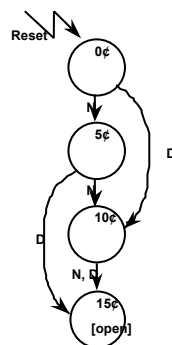

reuse states
whenever
possible

Present State	Inputs		Next State	Output Open
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	X	X
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	X	X
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	X	X
15¢	X	X	15¢	1

Symbolic State Table

16

Vending Machine Example

Step 4: State Encoding



Present State Inputs				Next State		Output
Q_1	Q_0	D	N	D_1	D_0	Open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	X	X	X
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	X	X	X
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	X	X	X
1	1	0	0	1	1	1
		0	1	1	1	1
		1	0	1	1	1
		1	1	X	X	X

17

Vending Machine Example

Step 5. Choose FFs for implementation

D FF easiest to use

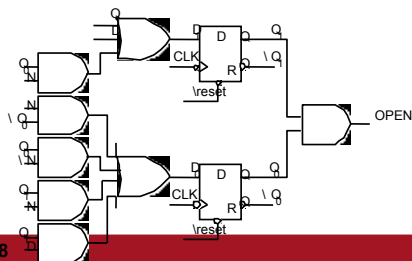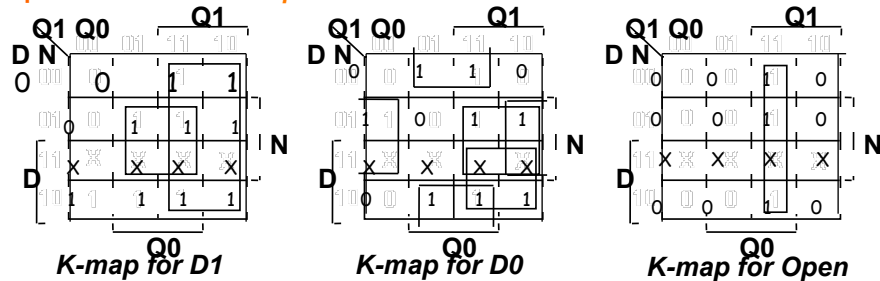


$$D_1 = Q_1 + D + Q_0 N$$

$$D_0 = N \bar{Q}_0 + Q_0 \bar{N} + Q_1 N + Q_1 D$$


$$OPEN = Q_1 Q_0$$

18

Moore Machine Block Diagram

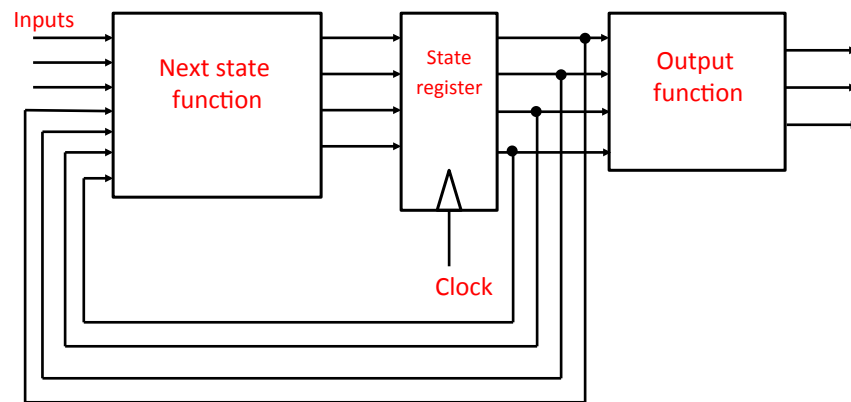

Mealy Machine Block Diagram

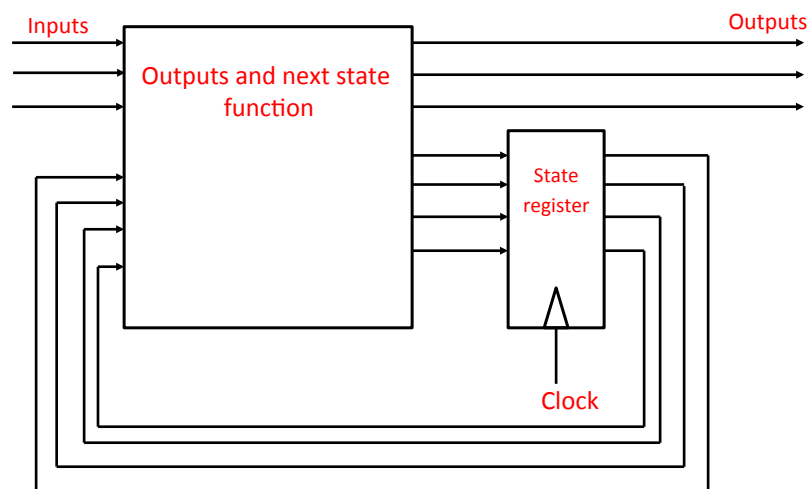

Basic Design Approach

1. Understand the statement of the Specification
2. Obtain an abstract specification of the FSM
3. Perform a state minimization
4. Perform state assignment
5. Choose FF types to implement FSM state register
6. Implement the FSM

21